 


**Lecture 10**  
**Digital Logic Design**  
**-- Basics**



# Logic Design


---

- From now, we'll study how a modern processor is built starting with basic logic elements as building blocks.
- Why study logic design?
  - Understand what processors can do fast and what they can't do fast (avoid slow things if you want your code to run fast!)
  - Background for more detailed hardware courses
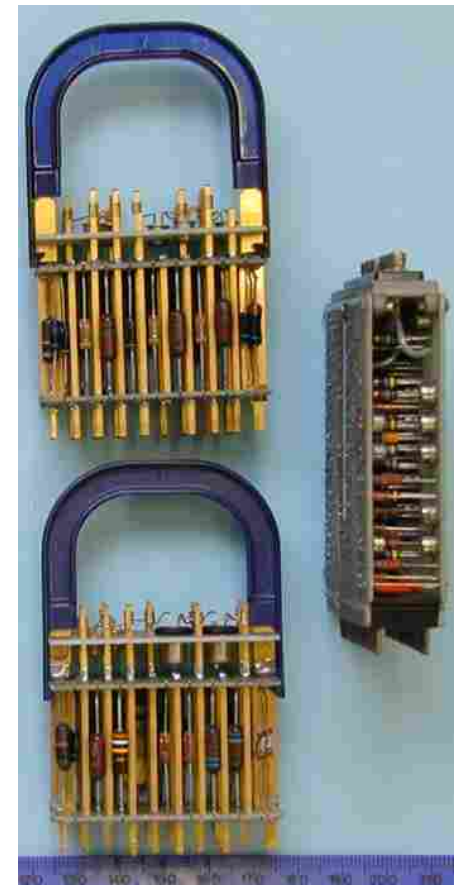
# Logic Gates


---

- Basic building blocks are logic *gates*.
  - In the beginning, did ad hoc designs, and then saw patterns repeated, gave names
  - Can build gates with transistors and resistors
- Then found theoretical basis for design
  - Can represent and reason about gates with truth tables and Boolean algebra
  - Assume know truth tables and Boolean algebra from a math or circuits course.
  - Section B.2 in the textbook has a review




# Gates


---

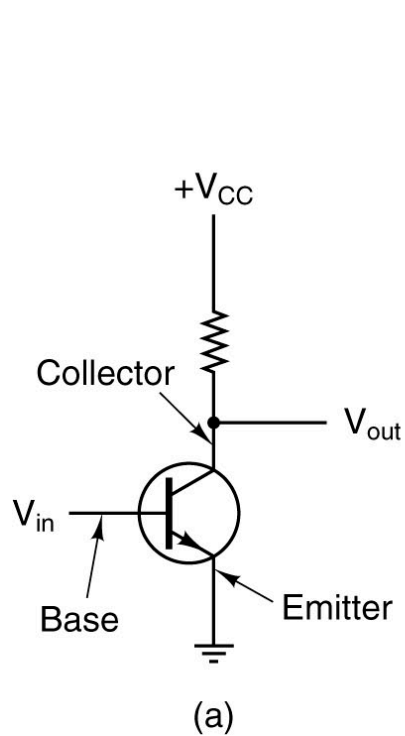

A transistor inverter  
or A NOT gate

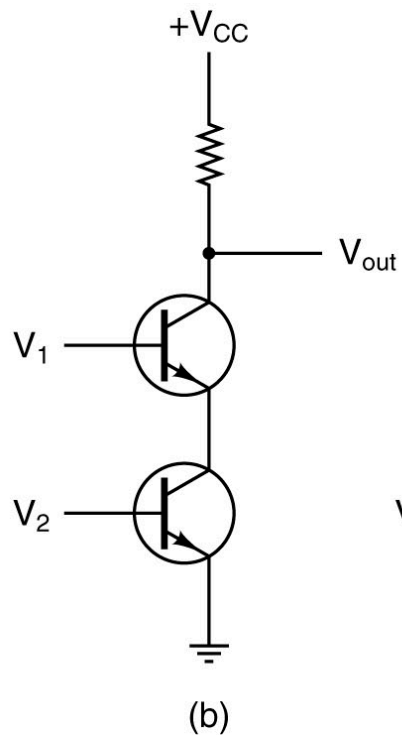

A NAND gate

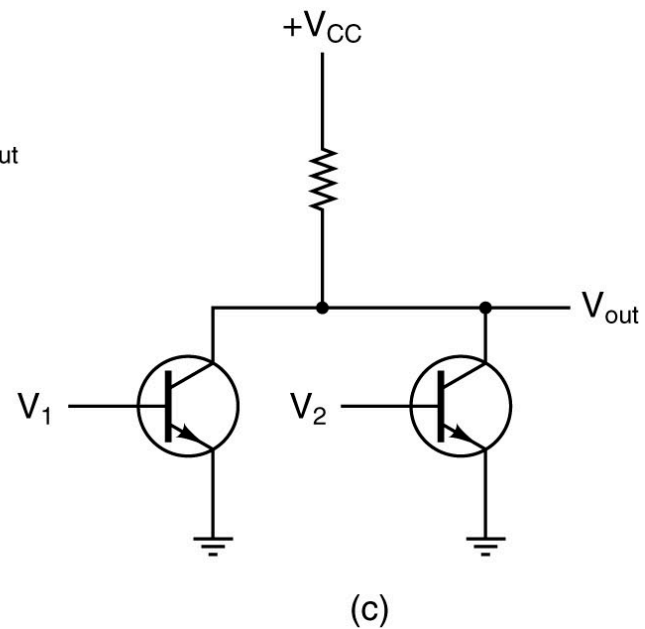


A NOR gate

# Gates and Boolean Algebra


---

## Five basic gates

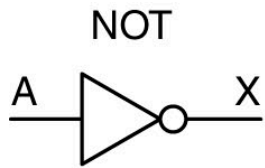


A	X
0	1
1	0

(a)

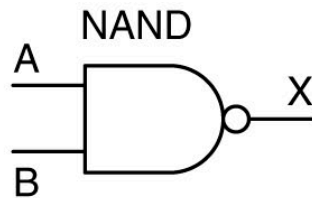


A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

(b)

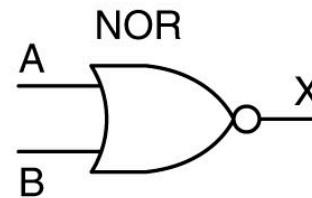


A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

(c)

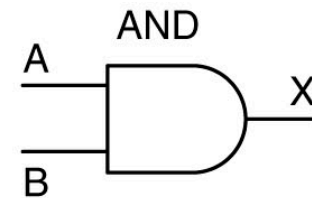

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

(d)

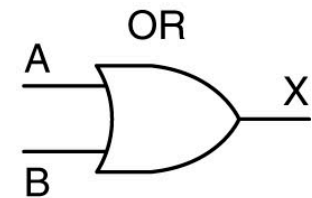

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

(e)

**Truth Table**

# Digit Display

---

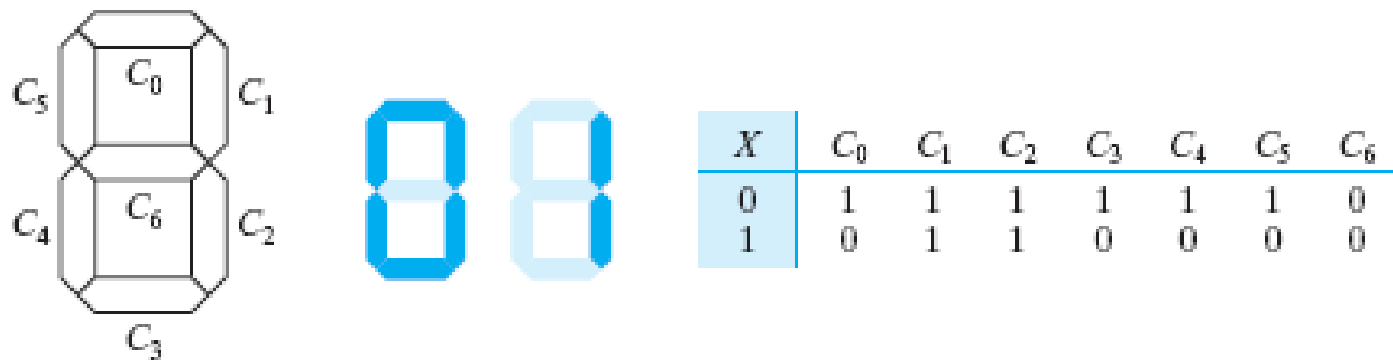


Figure 2.4 Binary digit-display combinational system.

# Building a Circuit

---

$$C_{\text{out}} = \bar{A}BC_{\text{in}} + A\bar{B}C_{\text{in}} + AB\bar{C}_{\text{in}} + ABC_{\text{in}}$$

- Use And/Or gates to implement this expression
- How many gates do we use?
- Can we use less


$$= BC_{\text{in}} + AC_{\text{in}} + AB(\bar{C}_{\text{in}} + C_{\text{in}})$$

$$= BC_{\text{in}} + AC_{\text{in}} + AB(1)$$

$$= BC_{\text{in}} + AC_{\text{in}} + AB$$

# **Boolean Algebra 101**

**How to simplify Boolean expression?**

 



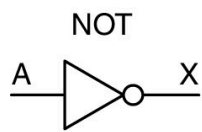
# Boolean Algebra (I)


---

- Using just '0' and '1's (after George Boole)
- Truth Table
  - A Boolean function with  $n$  variables has only  $2^n$  possible input combinations
  - A table with  $2^n$  rows




A	X
0	1
1	0

(a)

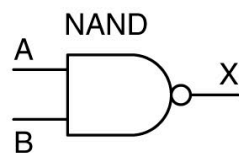


A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

(b)

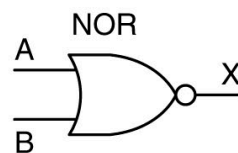


A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

(c)

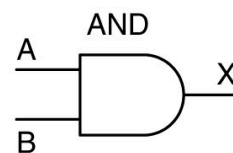

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

(d)

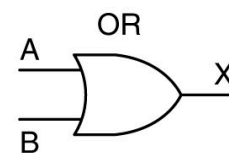


A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

(e)

# Boolean Algebra (2)


---

## ■ Algebra representations

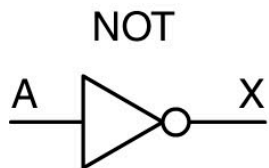


A	X
0	1
1	0

(a)

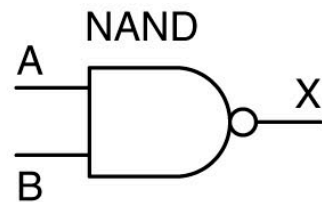


A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

(b)

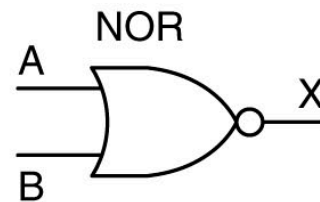


A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

(c)

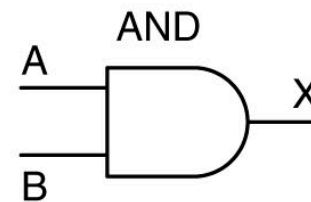

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

(d)

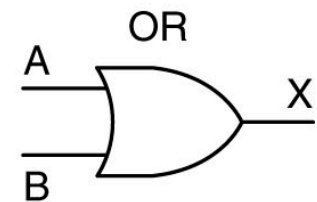

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1


(e)

# Boolean Algebra (3)

Another example with 3 inputs

A	B	C	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(a)

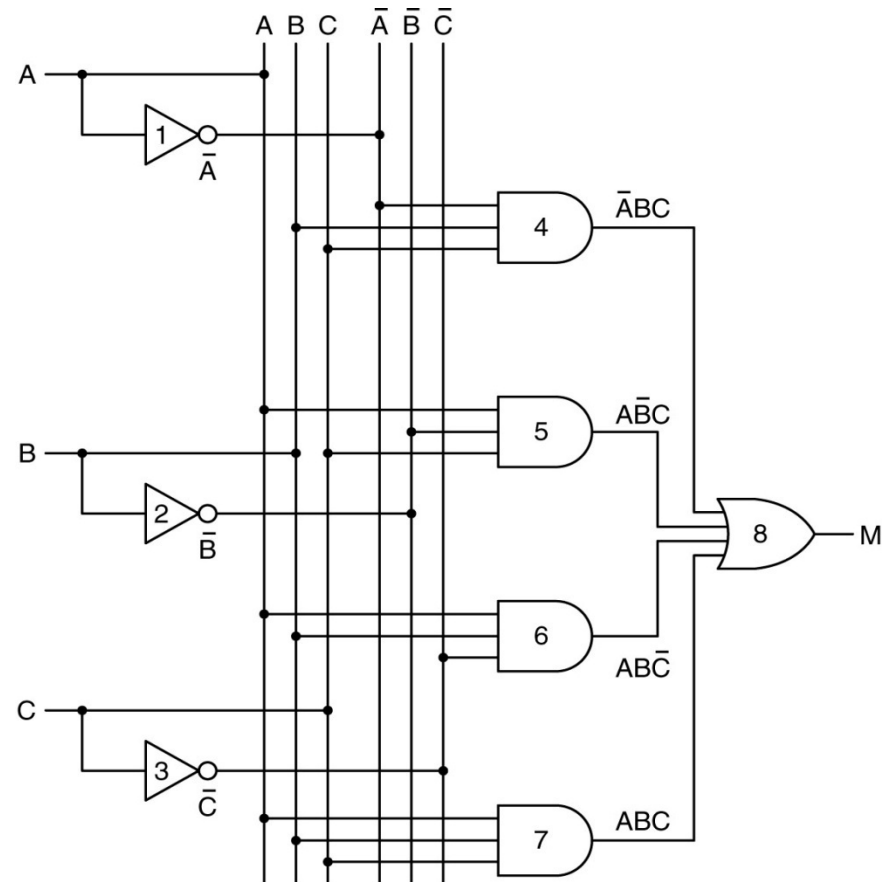

(b)

# Boolean Algebra (4)

---

- All Boolean functions can be implemented by logic gates (AND, OR, NOT) and vice versa.

- Boolean operations

- AND:  $XY$ ,  $X \wedge Y$ ,  $X \& Y$

- OR:  $X+Y$ ,  $X \vee Y$ ,  $X | Y$

- NOT:  $\bar{X}$ ,  $X'$ ,  $/X$ ,  $\backslash X$

$$\bar{A} \cdot B + C = ((\bar{A}) \cdot B) + C$$

$$\bar{A} + B \cdot C = (\bar{A}) + (B \cdot C)$$

- Order: NOT, AND, OR

# Basics

---

- P1:  $X = 0$  or  $X = 1$
- P2:  $0 \cdot 0 = 0$
- P3:  $1 + 1 = 1$
- P4:  $0 + 0 = 0$
- P5:  $1 \cdot 1 = 1$
- P6:  $1 \cdot 0 = 0 \cdot 1 = 0$
- P7:  $1 + 0 = 0 + 1 = 1$

# Boolean Laws

---

- T1 : Commutative Law

- $A + B = B + A$

- $A B = B A$

- T2 : Associate Law

- $(A + B) + C = A + (B + C)$

- $(A B) C = A (B C)$

# Boolean Laws

---

- T3 : Distributive Law

- $A (B + C) = A B + A C$

- $A + (B C) = (A + B) (A + C)$

- T4 : Identity Law

- $A + A = A$

- $A A = A$

# Laws

---

- T6 : Redundancy Law

- $A + A B = A$
- $A (A + B) = A$

- T7

- $0 + A = A$
- $0 A = 0$

- T8

- $1 + A = 1$
- $1 A = A$



# Other Laws

Name	AND form	OR form
Identity law	$1A = A$	$0 + A = A$
Null law	$0A = 0$	$1 + A = 1$
Idempotent law	$AA = A$	$A + A = A$
Inverse law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative law	$AB = BA$	$A + B = B + A$
Associative law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive law	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption law	$A(A + B) = A$	$A + AB = A$
De Morgan's law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}\bar{B}$

# Example

---

$$\begin{aligned}C_{\text{out}} &= \bar{A}BC_{\text{in}} + A\bar{B}C_{\text{in}} + AB\bar{C}_{\text{in}} + ABC_{\text{in}} \\&= \bar{A}BC_{\text{in}} + A\bar{B}C_{\text{in}} + AB\bar{C}_{\text{in}} + ABC_{\text{in}} + ABC_{\text{in}} \\&= \bar{A}BC_{\text{in}} + ABC_{\text{in}} + A\bar{B}C_{\text{in}} + AB\bar{C}_{\text{in}} + ABC_{\text{in}} \\&= (\bar{A} + A)BC_{\text{in}} + A\bar{B}C_{\text{in}} + AB\bar{C}_{\text{in}} + ABC_{\text{in}} \\&= (1)BC_{\text{in}} + A\bar{B}C_{\text{in}} + AB\bar{C}_{\text{in}} + ABC_{\text{in}} \\&= BC_{\text{in}} + A\bar{B}C_{\text{in}} + AB\bar{C}_{\text{in}} + ABC_{\text{in}} \\&= BC_{\text{in}} + AC_{\text{in}} + AB(\bar{C}_{\text{in}} + C_{\text{in}}) \\&= BC_{\text{in}} + AC_{\text{in}} + AB(1) \\&= BC_{\text{in}} + AC_{\text{in}} + AB\end{aligned}$$

**Idempotent theorem +  
commutative law**

**distributive law**

**complementarity law**

**identity law**

# Question 1

---

Simplify the Boolean expression

$(A+B+C)(D+E)' + (A+B+C)(D+E)$  and choose the best answer.

- $A + B + C$
- $D + E$
- $A'B'C'$
- $D'E'$
- None of the above

## Question 2

---

Given the function  $F(X,Y,Z) = XZ + Z(X' + XY)$ , the equivalent most simplified Boolean representation for F is:

- $Z + YZ$
- $Z + XYZ$
- $XZ$
- $X + YZ$
- None of the above

## Question 3

---

An equivalent representation for the Boolean expression  $A' + 1$  is

- $A$
- $A'$
- $1$
- $0$

## Question 4

---

Simplification of the Boolean expression

$AB + ABC + ABCD + ABCDE + ABCDEF$

yields which of the following results?

- $ABCDEF$
- $AB$
- $AB + CD + EF$
- $A + B + C + D + E + F$
- $A + B(C+D(E+F))$

## Question 5

---

Given that  $F = A'B' + C' + D' + E'$ , which of the following represent the only correct expression for  $F'$ ?

- $F' = A + B + C + D + E$
- $F' = ABCDE$
- $F' = AB(C + D + E)$
- $F' = AB + C' + D' + E'$
- $F' = (A + B)CDE$

# Deriving Complement of a Boolean Expression

---

- DeMorgan's LAW: **The complement of a Boolean expression is formed by replacing all literals by their compliments; ANDs become ORs, ORs become ANDs**

$$\overline{X + Y} = \bar{X} \cdot \bar{Y}$$

$$\overline{X \cdot Y} = \bar{X} + \bar{Y}$$



## Using DeMorgan's Law



$$\overline{X + Y} = \bar{X} \cdot \bar{Y}$$

$$\overline{X \cdot Y} = \bar{X} + \bar{Y}$$

$$\overline{X + Y \cdot Z} = ?$$

## Question 5

---

Given that  $F = A'B' + C' + D' + E'$ , which of the following represent the only correct expression for  $F'$ ?

- $F' = A + B + C + D + E$
- $F' = ABCDE$
- $F' = AB(C + D + E)$
- $F' = AB + C' + D' + E'$
- $F' = (A + B)CDE$

## Question 6

---

Given the function  $F(A,B,X,Y) = AB + X'Y$ , the most simplified Boolean representation for  $F'$  is

- $(AB)' + (X'Y)$
- $A'B' + XY'$
- $(A' + B')(X + Y')$
- $(AB + X'Y)'$
- $(AB)'(X'Y)'$

## Question 7

---

Given the function  $F(X,Y,Z) = XZ + Z(X' + XY)$ , the equivalent, most simplified Boolean representation for F is

- $Z + YZ$
- $Z + XYZ$
- $XZ$
- $Z$
- none of the above

## Question 8

---

Simplification of the Boolean expression  $AB + A(BC)'$  yields which of following results?

- A
- BC
- B
- AB
- $(BC)'$