

Answers to Exercises in Quantum Computation I

Wim van Dam

Department of Computer Science, University of California at Santa Barbara, Santa Barbara, CA 93106-5110, USA

Answer 1 (Analyzing Small Circuits).

(a) The circuit consists of four sequential transformations of 2 qubits, with the corresponding matrices:

$$I \otimes X = \begin{pmatrix} 0 & 1 & 0 & 0 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{pmatrix}$$

$$H \otimes H = \frac{1}{2} \begin{pmatrix} +1 & +1 & +1 & +1 \\ +1 & -1 & +1 & -1 \\ +1 & +1 & -1 & -1 \\ +1 & -1 & -1 & +1 \end{pmatrix}$$

$$\text{CNOT} = \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{pmatrix}$$

and again the matrix of $H \otimes H$.

The effect of this circuit on a 2 qubit state $|\psi\rangle$ is described by $(H \otimes H)(\text{CNOT})(H \otimes H)(I \otimes X)|\psi\rangle$, which shows why the transformation matrix of this circuit equals

$$M_{\text{circuit}} = \begin{pmatrix} 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 0 \end{pmatrix}$$

As a result, the behavior of the circuit on the four classical basis states is:

$ a, b\rangle$	$M_{\text{circuit}} a, b\rangle$
$ 0, 0\rangle$	$ 1, 1\rangle$
$ 0, 1\rangle$	$ 0, 0\rangle$
$ 1, 0\rangle$	$ 0, 1\rangle$
$ 1, 1\rangle$	$ 1, 0\rangle$

(b) This circuit has the following effect on the four basis states


input	output
$ 0, 0\rangle$	$ 0, 0\rangle$
$ 0, 1\rangle$	$ 0, 1\rangle$
$ 1, 0\rangle$	$ 1, 0\rangle$
$ 1, 1\rangle$	$- 1, 1\rangle$

hence its matrix representation is

$$\begin{pmatrix} +1 & 0 & 0 & 0 \\ 0 & +1 & 0 & 0 \\ 0 & 0 & +1 & 0 \\ 0 & 0 & 0 & -1 \end{pmatrix}$$

Answer 2 (Designing Small Circuits).

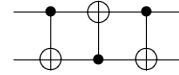
(a) The following circuit implements the SWAP gate



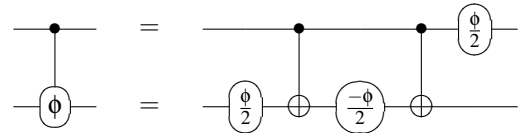(b) From now on we denote the single qubit phase rotation gate by the circuit element

$$\begin{pmatrix} 1 & 0 \\ 0 & e^{i\phi} \end{pmatrix} \cong \text{---} \bigcirc_{\phi} \text{---}$$


We can implement the controlled phase rotation by



Answer 3 (Controlled NOTs).

(a) It is not possible to implement a CCNOT gate using CNOT gates. Let $a, b, c \in \{0, 1\}$ be the 3 bits input of a CNOT circuit. Describe the effect of the circuit on the third qubit as a mod 2 calculation such that CCNOT with its $|a, b, c\rangle \mapsto |a, b, c + ab\rangle$ is viewed as a second degree polynomial (because of the product term ab). As the CNOT gate with its mapping $|a, b\rangle \mapsto |a, b \oplus a\rangle$ will only produce linear functions in a, b, c , a CNOT circuit is not capable of implementing a CCNOT gate.

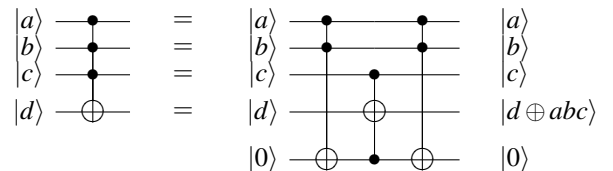(b) It is possible to implement a CCCNOT gate using CCNOT gates as the following circuit shows



Note how we drew the CCNOT gates here: The first CCNOT gate has as control bits $|a\rangle$ and $|b\rangle$, while $|c\rangle$ and $|d\rangle$ do not play a role, which is indicated by the solid control dots on the relevant wires.

Answer 4 (Unitarity). Consider the effect of T on the vector $|\psi\rangle - |\phi\rangle$. Because $|\psi\rangle \neq |\phi\rangle$ we have $\| |\psi\rangle - |\phi\rangle \| \neq 0$. On the other hand, because T is linear, it must hold that $\| T(|\psi\rangle - |\phi\rangle) \| = \| |0, \dots, 0\rangle - |0, \dots, 0\rangle \| = 0$. Hence T is not norm preserving.

Acknowledgment: Again, the circuits in these exercises were drawn using the Q-circuit \LaTeX package of Bryan Eastin and Steven T. Flammia.