

Answers to Exercises in Quantum Computation II


Wim van Dam

Department of Computer Science, University of California at Santa Barbara, Santa Barbara, CA 93106-5110, USA

Answer 1. (The Effect of Pauli Gates). The following table describes the effect of the X -gate on the output state.


? -gate	I	X	Y	Z
Output	$ 0,0\rangle$	$ 0,1\rangle$	$-i 1,1\rangle$	$ 1,0\rangle$

Answer 2. (Creating Correlated Quantum States). The following circuit creates the required superposition $\frac{1}{\sqrt{2}}(|0,0,0,0\rangle + |1,1,1,1\rangle)$.

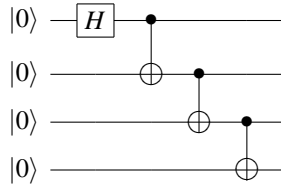


Answer 3. (Implementing Modulo Calculations).

(a) Because $a + b = 2(a_1 + b_1) + (a_0 + b_0)$, we have to implement the 6 bit operation $|a_1, a_0, b_1, b_0, 0, 0\rangle \mapsto |a_1, a_0, b_1, b_0, a_1 + b_1 + a_0 b_0, a_0 + b_0\rangle$, where the additions and multiplications are done mod 2.

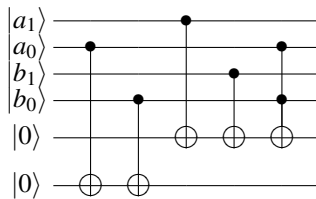


(b) Because $ab = 4a_1b_1 + 2(a_1b_0 + a_0b_1) + a_0b_0 = 2(a_1b_0 + a_0b_1) + a_0b_0 \pmod 4$, we have to implement the 6 bit operation $|a_1, a_0, b_1, b_0, 0, 0\rangle \mapsto |a_1, a_0, b_1, b_0, a_1b_0 + a_0b_1, a_0b_0\rangle$, where the additions and multiplications are done mod 2.

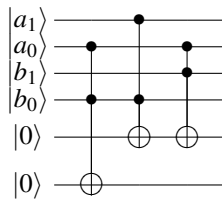

(c) Write the numbers as $a = \sum_{j=0}^{n-1} a_j 2^j$ and $b = \sum_{j=0}^{n-1} b_j 2^j$ such that $a + b = \sum_{j=0}^{n-1} (a_j + b_j) 2^j$ and $ab = \sum_{j=0}^{n-1} (a_0 b_j + \dots + a_j b_0) 2^j$. Use extra bits to implement the carry bits when adding or multiplying the numbers a and b . These techniques are well-known from traditional circuit complexity.

Answer 4. (Copying Qubits).

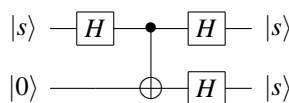(a) Use the following circuit for all $s \in \{-, +\}$



(b) The effect of this circuit on the states $|b,0\rangle$ is $|0,0\rangle \mapsto \frac{1}{\sqrt{2}}(|0,0\rangle + |1,1\rangle)$ and $|1,0\rangle \mapsto \frac{1}{\sqrt{2}}(|0,1\rangle + |1,0\rangle)$.

(c) (Proof by contradiction.) Let $U \in \mathbb{C}^{4 \times 4}$ be the unitary matrix of the 2 qubit circuit. Because of the requirement $U : |0,0\rangle \mapsto |0,0\rangle$ the first column of the matrix U must have the form

$$\begin{pmatrix} 1 & * & * & * \\ 0 & * & * & * \\ 0 & * & * & * \\ 0 & * & * & * \end{pmatrix} \begin{pmatrix} 1 \\ 0 \\ 0 \\ 0 \end{pmatrix} = \begin{pmatrix} 1 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

Next, because of the other requirement $U : |+,0\rangle \mapsto |+,+\rangle$ the third column of U must have the form

$$\begin{pmatrix} 1 & * & \frac{1}{\sqrt{2}} & -1 & * \\ 0 & * & \frac{1}{\sqrt{2}} & * & * \\ 0 & * & \frac{1}{\sqrt{2}} & * & * \\ 0 & * & \frac{1}{\sqrt{2}} & * & * \end{pmatrix} \begin{pmatrix} \frac{1}{\sqrt{2}} \\ 0 \\ \frac{1}{\sqrt{2}} \\ 0 \end{pmatrix} = \frac{1}{2} \begin{pmatrix} 1 \\ 1 \\ 1 \\ 1 \end{pmatrix}$$

Thus the first and the third column of U are not orthogonal, hence U is not unitary.

Alternatively, we can prove the nonunitarity of U as follows. We have $\langle 0,0|+,0\rangle = \frac{1}{\sqrt{2}} \neq \frac{1}{2} = \langle 0,0|+,+\rangle$, hence this U can not be inner-product preserving.

Answer 5. (Exploring an Unknown Function).

(a) Depending on the two values $f(0)$ and $f(1)$ the output states are as follows

$f(0)$	$f(1)$	output state
0	0	$\frac{1}{2}(+\rangle 0\rangle + +\rangle 1\rangle) \otimes (0\rangle - 1\rangle)$
0	1	$\frac{1}{2}(+\rangle 0\rangle - +\rangle 1\rangle) \otimes (0\rangle - 1\rangle)$
1	0	$\frac{1}{2}(-\rangle 0\rangle + -\rangle 1\rangle) \otimes (0\rangle - 1\rangle)$
1	1	$\frac{1}{2}(-\rangle 0\rangle - -\rangle 1\rangle) \otimes (0\rangle - 1\rangle)$

(b) If you apply a Hadamard on the first qubit and then measure it in the computational basis, then you will see a “0” if and only if $f(0) = f(1)$ and you will see a “1” if and only if $f(0) \neq f(1)$. Note that this quantum procedure can therefore decide the question $f(0) = f(1)$? with only one query to f .

Acknowledgment: Again, the circuits in these exercises were drawn using the Q-circuit \LaTeX package of Bryan Eastin and Steven T. Flammia.