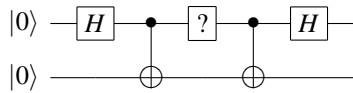


## Exercises in Quantum Computation II v2

Wim van Dam

*Department of Computer Science, University of California at Santa Barbara, Santa Barbara, CA 93106-5110, USA*

**Question 1.** (The Effect of Pauli Gates). Consider the following 2 qubit circuit:



where the ?-gate can be one of the Pauli matrices  $\{I, X, Y, Z\}$ . Calculate what the output of this quantum circuit will be depending on the choice for the ?-gate.

**Question 2.** (Creating Correlated Quantum States). Describe a 4 qubit circuit that from the input  $|0, 0, 0, 0\rangle$  produces the state  $\frac{1}{\sqrt{2}}(|0, 0, 0, 0\rangle + |1, 1, 1, 1\rangle)$ .

**Question 3.** (Implementing Modulo Calculations). We are going to implement mod4 calculations in a unitary (and hence reversible) way. Let  $a = (a_1, a_0)$  and  $b = (b_1, b_0)$  represent two numbers  $\in \mathbb{Z}_4$  according to  $a = 2a_1 + a_0$  and  $b = 2b_1 + b_0$ . You are allowed to use all the standard gates.

- (a) Describe a small 6 qubit circuit that implements the addition transformation  $|a, b, 0\rangle \mapsto |a, b, a + b \bmod 4\rangle$ .
- (b) Describe a small qubit circuit that implements the multiplication transformation  $|a, b, 0\rangle \mapsto |a, b, ab \bmod 4\rangle$ .
- (c) Contemplate how well you can generalize this to  $n$  bits numbers  $a, b \in \mathbb{Z}_{2^n}$ .

**Question 4.** (Copying Qubits). Notation: We define the qubit states  $|+\rangle := \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle)$  and  $|-\rangle := \frac{1}{\sqrt{2}}(|0\rangle - |1\rangle)$ .

- (a) The CNOT gate copies the bit value  $b$  in the operation  $|b, 0\rangle \mapsto |b, b\rangle$  for all  $b \in \{0, 1\}$ . Describe a quantum circuit that copies the states  $\{|+\rangle, |-\rangle\}$ . That is: give a circuit that implements the mapping  $|s, 0\rangle \mapsto |s, s\rangle$  for all  $s \in \{+, -\}$ .
- (b) Describe the effect of the circuit of the previous question on the states  $|b, 0\rangle$  for all  $b \in \{0, 1\}$ .
- (c) Prove that there exists no quantum circuit that implements a 2 qubit operation with the mappings  $|0, 0\rangle \mapsto |0, 0\rangle$  and  $|+, 0\rangle \mapsto |+, +\rangle$ . If possible, try to find more than one proof.

**Question 5.** (Exploring an Unknown Function). Take a Boolean function  $f : \{0, 1\} \rightarrow \{0, 1\}$  and define its 2 qubit unitary implementation  $U_f : |a, b\rangle \mapsto |a, b \oplus f(a)\rangle$ .

- (a) Apply this  $U_f$  to the superposition  $\frac{1}{2}(|0\rangle + |1\rangle) \otimes (|0\rangle - |1\rangle)$  and see what happens to the two qubits depending on the function values  $f(0)$  and  $f(1)$ .
- (b) Ponder what you could do with the result of the previous question if you were allowed to apply some Hadamard gates after the application of  $U_f$ .

**Acknowledgment:** Again, the circuits in these exercises were drawn using the Q-circuit  $\LaTeX$  package of Bryan Eastin and Steven T. Flammia.