

# Answers to Exercises in Quantum Computation II

Wim van Dam


*Departments of Computer Science and Physics, University of California at Santa Barbara, Santa Barbara, CA 93106-5110, USA*

Answers to the Exercises II for the course “Quantum Computation and Quantum Information”, Spring 2007.

**Question 1.** (The Effect of Pauli Gates). The following table describes the effect of the ?-gate on the output state.


?-gate	$I$	$X$	$Y$	$Z$
Output	$ 0,0\rangle$	$ 0,1\rangle$	$-i 1,1\rangle$	$ 1,0\rangle$

**Question 2.** (Creating Correlated Quantum States). The following circuit creates the required superposition  $\frac{1}{\sqrt{2}}(|0,0,0,0\rangle + |1,1,1,1\rangle)$ .

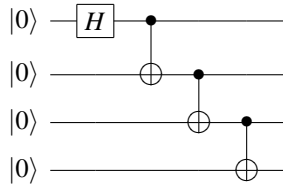


**Question 3.** (Implementing Modulo Calculations).

(a) Because  $a + b = 2(a_1 + b_1) + (a_0 + b_0)$ , we have to implement the 6 bit operation  $|a_1, a_0, b_1, b_0, 0, 0\rangle \mapsto |a_1, a_0, b_1, b_0, a_1 + b_1 + a_0 b_0, a_0 + b_0\rangle$ , where the additions and multiplications are done mod 2.

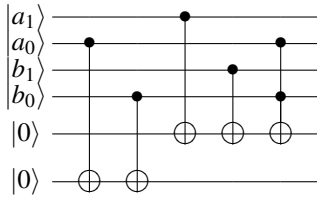


(b) Because  $ab = 4a_1b_1 + 2(a_1b_0 + a_0b_1) + a_0b_0 = 2(a_1b_0 + a_0b_1) + a_0b_0 \pmod 4$ , we have to implement the 6 bit operation  $|a_1, a_0, b_1, b_0, 0, 0\rangle \mapsto |a_1, a_0, b_1, b_0, a_1b_0 + a_0b_1, a_0b_0\rangle$ , where the additions and multiplications are done mod 2.

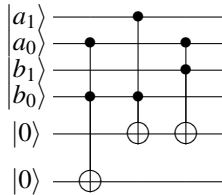

(c) Write the numbers as  $a = \sum_{j=0}^{n-1} a_j 2^j$  and  $b = \sum_{j=0}^{n-1} b_j 2^j$  such that  $a + b = \sum_{j=0}^{n-1} (a_j + b_j) 2^j$  and  $ab = \sum_{j=0}^{n-1} (a_0 b_j + \dots + a_j b_0) 2^j$ . Use extra bits to implement the carry bits when adding or multiplying the numbers  $a$  and  $b$ . These techniques are well-known from traditional circuit complexity.

**Question 4.** (Copying Qubits).

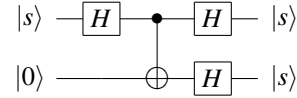(a) Use the following circuit for all  $s \in \{-, +\}$



(b) The effect of this circuit on the states  $|b,0\rangle$  is  $|0,0\rangle \mapsto \frac{1}{\sqrt{2}}(|0,0\rangle + |1,1\rangle)$  and  $|1,0\rangle \mapsto \frac{1}{\sqrt{2}}(|0,1\rangle + |1,0\rangle)$ .

(c) (Proof by contradiction.) Let  $U \in \mathbb{C}^{4 \times 4}$  be the unitary matrix of the 2 qubit circuit. Because of the requirement  $U : |0,0\rangle \mapsto |0,0\rangle$  the first column of the matrix  $U$  must have the form

$$\begin{pmatrix} 1 & * & * & * \\ 0 & * & * & * \\ 0 & * & * & * \\ 0 & * & * & * \end{pmatrix} \begin{pmatrix} 1 \\ 0 \\ 0 \\ 0 \end{pmatrix} = \begin{pmatrix} 1 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

Next, because of the other requirement  $U : |+,0\rangle \mapsto |+,+\rangle$  the third column of  $U$  must have the form

$$\begin{pmatrix} 1 & * & \frac{1}{\sqrt{2}} - 1 & * \\ 0 & * & \frac{1}{\sqrt{2}} & * \\ 0 & * & \frac{1}{\sqrt{2}} & * \\ 0 & * & \frac{1}{\sqrt{2}} & * \end{pmatrix} \begin{pmatrix} \frac{1}{\sqrt{2}} \\ 0 \\ \frac{1}{\sqrt{2}} \\ 0 \end{pmatrix} = \frac{1}{2} \begin{pmatrix} 1 \\ 1 \\ 1 \\ 1 \end{pmatrix}$$

Thus the first and the third column of  $U$  are not orthogonal, hence  $U$  is not unitary.

Alternatively, we can prove the nonunitarity of  $U$  as follows. We have  $\langle 0,0|+,0\rangle = \frac{1}{\sqrt{2}} \neq \frac{1}{2} = \langle 0,0|+,+\rangle$ , hence this  $U$  can not be inner-product preserving.

**Question 5.** (Exploring an Unknown Function).

(a) Depending on the two values  $f(0)$  and  $f(1)$  the output states are as follows

$f(0)$	$f(1)$	output state
0	0	$\frac{1}{2}( +\rangle 0\rangle +  +\rangle 1\rangle) \otimes ( 0\rangle -  1\rangle)$
0	1	$\frac{1}{2}( +\rangle 0\rangle -  +\rangle 1\rangle) \otimes ( 0\rangle -  1\rangle)$
1	0	$\frac{1}{2}( -\rangle 0\rangle +  -\rangle 1\rangle) \otimes ( 0\rangle -  1\rangle)$
1	1	$\frac{1}{2}( -\rangle 0\rangle -  -\rangle 1\rangle) \otimes ( 0\rangle -  1\rangle)$

(b) If you apply a Hadamard on the first qubit and then measure it in the computational basis, then you will see a “0” if and only if  $f(0) = f(1)$  and you will see a “1” if and only if  $f(0) \neq f(1)$ . Note that this quantum procedure can therefore decide the question  $f(0) = f(1)$ ? with only one query to  $f$ .

**Acknowledgment:** Again, the circuits in these exercises were drawn using the Q-circuit  $\LaTeX$  package of Bryan Eastin and Steven T. Flammia.